

FPGA BASED SYSTEM DESIGN

Dr. Tayab Din Memon

tayabuddin.memon@faculty.muet.edu.pk

Lecture 9 & 10 : Combinational and Sequential
Logic

Combinational vs Sequential Logic

- Combinational logic output depends upon the current input
 - Memory less system
- Sequential logic output needs memory because it depends upon the previous states
 - Storage elements connected in feedback loop with combinational logic

 


Figure (1)

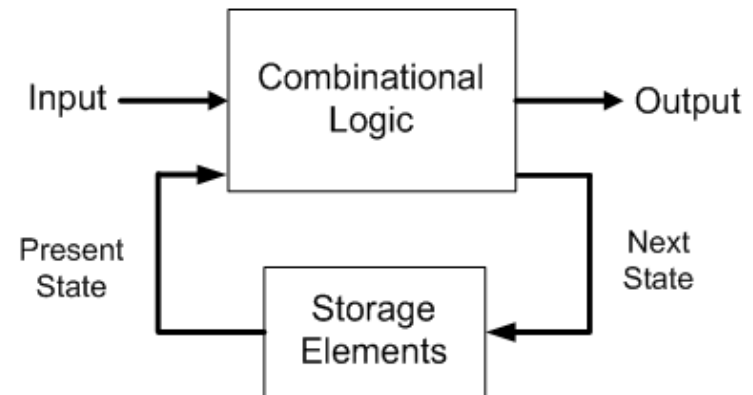


Figure (2)

 


Figure (3)

Concurrent vs Sequential Code

- Only statements placed inside
 - the process
 - the procedure
 - or function are sequential
 - but VHDL code is inherently concurrent (parallel)
- In other words, concurrent are
 - Statements *outside of a process*
 - Processes are evaluated concurrently
- Concurrent code is also called *dataflow code*
- In general combinational logic circuits are build with concurrent code

stat1 stat3 stat1
stat2 ≡ stat2 ≡ stat3 ≡ etc
stat3 stat1 stat2

Concurrent Statements

- Concurrent statements include:
 - Boolean equations
 - conditional assignments (when/else, with/select)
 - instantiation

Using Operators

Operator Type	Operators	Data Types
Logical	NOT, AND, NAND, OR, XOR, NOR, XNOR	BIT, BIT_VECTOR, STD_LOGIC, STD_LOGIC_VECTOR, STD_ULOGIC, STD_ULOGIC_VECTOR
Arithmetic	+, -, *, /, **, MOD, REM, ABS	INTEGER, SIGNED, UNSIGNED
Comparison	=, /=, <, >, <=, >=	BIT, BIT_VECTOR, STD_LOGIC, STD_LOGIC_VECTOR, STD_ULOGIC, STD_ULOGIC_VECTOR, INTEGER, SIGNED, UNSIGNED
Shift	sll, srl, sla, sra, rol, ror	BIT_VECTOR
Concatenation	&, (,,)	Same as for logical operators, plus signed and unsigned

- Easiest and basic way of creating concurrent code
- Complex circuits are easier to deal with sequential code comparatively, infact

Example – I: Multiplexer

```
library ieee;
use ieee.std_logic_1164.all;

entity MUX_Test is
port (s,t,u,v,w,x: in std_logic;
      y: out std_logic);
end MUX_Test;

architecture dataflow of MUX_Test is
begin
  y<= (s and not x and not w) OR
      (t and not x and w) OR
      (u and x and not w) OR
      (v and x and w);
end dataflow;
```

 


Fig: MUX Block

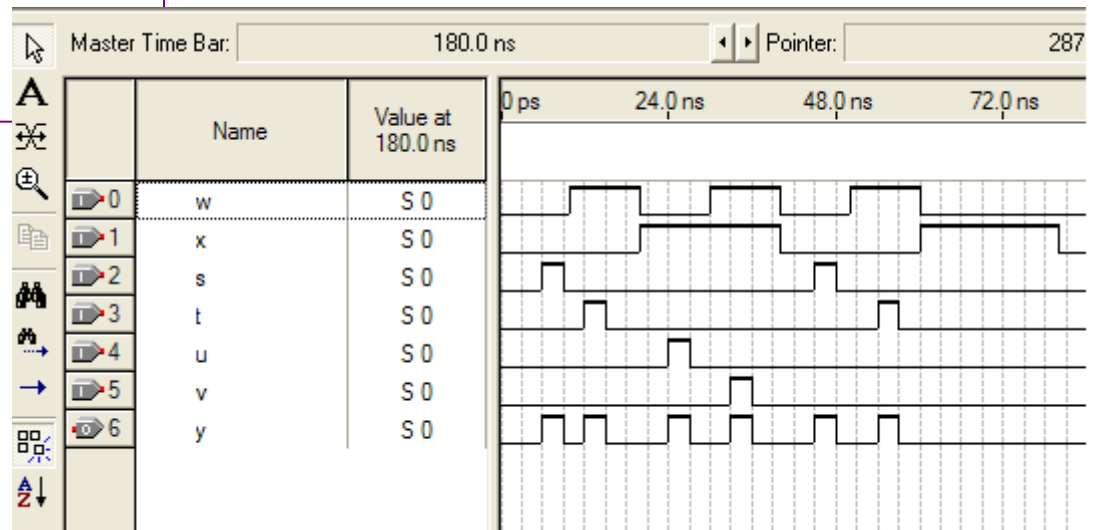


Fig: MUX

When Statement

Example: When/ Else or with/ Select / When

When/ Else or with/ Select / When Syntax

```
--WHEN / ELSE STATEMENT
```

```
assignment WHEN condition ELSE  
assignment WHEN condition ELSE  
....;
```

```
-- WITH/ SELECT / WHEN STATEMENT
```

```
WITH identifier SELECT  
assignment WHEN value,  
assignment WHEN value,  
....;
```

```
-- WHEN/ ELSE
```

```
y <= "00" WHEN (a = '0' or re='1')  
    else  
    "01" WHEN ena='1'  
    else  
    "10";
```

```
-- WITH / SELECT / WHEN
```

```
WITH control SELECT  
y <= "00" WHEN re  
    "01" WHEN ena  
    UNAFFECTED WHEN OTHERS;
```

```
WHEN value
```

```
WHEN value1 to value2
```

```
WHEN value1 | value2 | ...
```

Example – 2: Solution with WHEN/ELSE

 


Fig: MUX Example - II

```
Architecture dataflow of MUXAgain is
begin
y <= s WHEN X=0 ELSE
    t WHEN X=1 ELSE
    u WHEN X=2 ELSE
    v;
END dataflow;
```


If x is an integer i.e., x : in integer range 0 to 3;

```
--Solution - 1: with WHEN/ELSE
library ieee;
use ieee.std_logic_1164.all;

Entity MUXAgain is
port (s,t,u,v: in std_logic;
      x : in std_logic_vector(1 downto 0);
      y : out std_logic);
end MUXAgain;
```

```
Architecture dataflow of MUXAgain is
begin
y <= s WHEN X="00" ELSE
    t WHEN X="01" ELSE
    u WHEN X="10" ELSE
    v;
END dataflow;
```


Solution – 2: with WITH/SELECT/WHEN

 

```
Architecture dataflow of MUXAgain is
begin
WITH X SELECT
y <= s WHEN 0,
    t WHEN 1,
    u WHEN 2,
    v WHEN 3;
END dataflow;
```

```
--Solution -2: with WITH/SELECT/WHEN
```

```
library ieee;
use ieee.std_logic_1164.all;
```

```
Entity MUXAgain is
```

```
port (s,t,u,v: in std_logic;
      x : in std_logic_vector(1 downto 0);
      y : out std_logic);
end MUXAgain;
```


```
Architecture dataflow of MUXAgain is
```

```
begin
WITH x SELECT
y <= s WHEN "00",
    t WHEN "01",
    u WHEN "10",
    v WHEN OTHERS;
END dataflow;
```

 Example – 3: Tri-

```
library ieee;
use ieee.std_logic_1164.all;

Entity tri_state_use is
port (ena : in std_logic;
      x : in std_logic_vector (7 downto 0);
      y : out std_logic_vector (7 downto 0));
end tri_state_use;
architecture dataflow of tri_state_use is
begin
y<= x when (ena = '1') else
  (others => 'Z');
end dataflow;
```



A

Fig: Tri-State Buffer

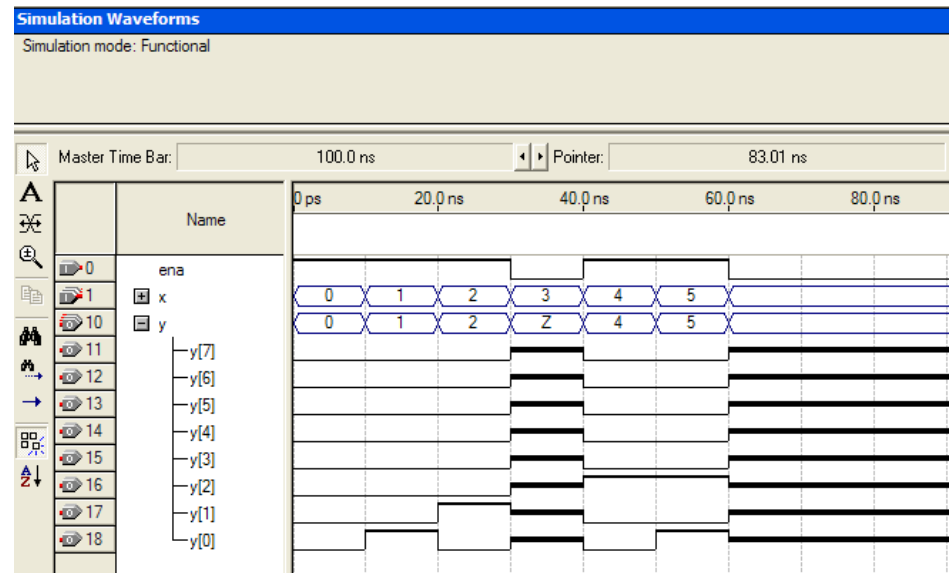


Fig: Vector Waveform

Encoder 8by3 (i.e., n=8, m=3) When-Else

```
library ieee;  
use ieee.std_logic_1164.all;  
  
Entity encoder8by3 is  
port (x : in std_logic_vector (7 downto 0);  
      y : out std_logic_vector (2 downto 0));  
end encoder8by3;
```

Architecture dataflow of encoder8by3 is

```
begin  
  y <= "000" WHEN X="00000001" ELSE  
       "001" WHEN X="00000010" ELSE  
       "010" WHEN X="00000100" ELSE  
       "011" WHEN X="00001000" ELSE  
       "100" WHEN X="00010000" ELSE  
       "101" WHEN X="00100000" ELSE  
       "110" WHEN X="01000000" ELSE  
       "111" WHEN X="10000000" ELSE  
       "ZZZ";  
END dataflow;
```

 


Fig: Encoder Block

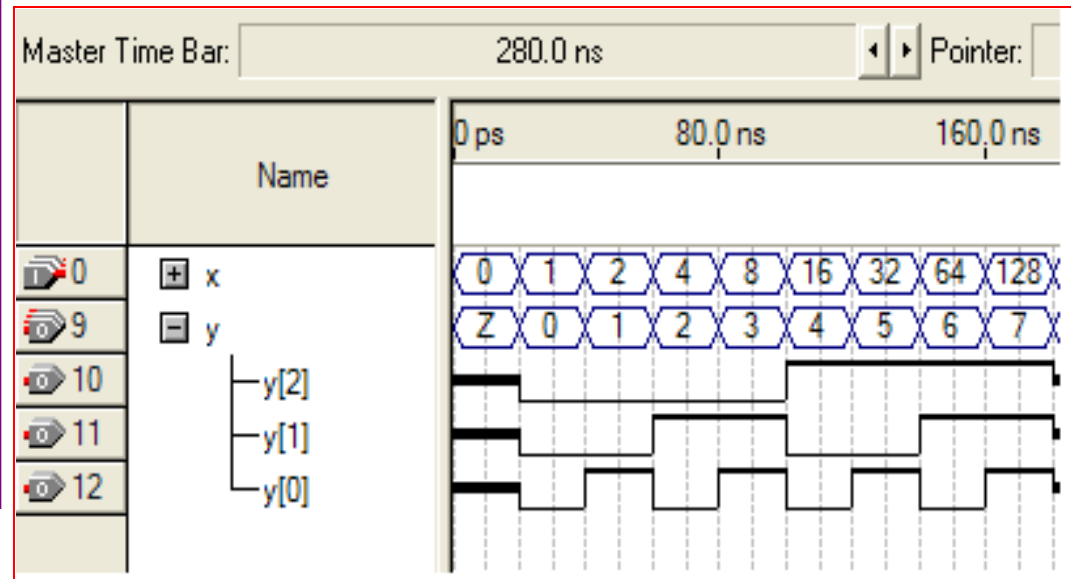


Fig: Simulation Results

Encoder 8by3 (i.e., n=8, m=3) With-Select-When

```
library ieee;
use ieee.std_logic_1164.all;

Entity encoder8by3_2 is
port (x : in std_logic_vector (7 downto 0);
      y : out std_logic_vector (2 downto 0));
end encoder8by3_2;

Architecture dataflow of encoder8by3_2 is
begin
  with x select
  y <= "000" WHEN "00000001",
      "001" WHEN "00000010",
      "010" WHEN "00000100",
      "011" WHEN "00001000",
      "100" WHEN "00010000",
      "101" WHEN "00100000",
      "110" WHEN "01000000",
      "111" WHEN "10000000",
      "ZZZ" WHEN OTHERS;
END dataflow;
```

GENERATE Statement

- It is another concurrent statement. It allows a section of code to be repeated a number of times, thus creating several instances of the same assignment.

```
label: FOR identifier IN range GENERATE  
  (concurrent assignments)  
ENG GENERATE;
```

- An irregular form of GENERATE statement is IF/GENERATE, syntax given below:

```
label: FOR identifier IN range GENERATE  
  .....  
  label2: IF condition GENERATE  
    (concurrent assignments)  
  end GENERATE;  
  ....  
end GENERATE;
```

How to use GENERATE Statement?

```
signal a: bit_vector (7 downto 0);  
signal b: bit_vector (15 downto 0);  
signal c: bit_vector (7 downto 0);  
  
.....  
  
D: FOR i in a'range generate  
    c(i) <= a(i) AND b(i+8);  
end generate;
```

```
g: FOR i IN 0 to input generate  
    (concurrent statement)  
end generate;
```

Example: input as variable

GENERATE Syntax – I

```
right: FOR i in 0 to 7 generate  
    outcome(i) <= '1' when (a(i) and b(i)) = '1' else '0';  
end generate;
```

Example: outcome as single driven

```
wrong: FOR i in 0 to 7 generate  
    outcome <= "11111111" when (a(i) and b(i))='1' else "00000000";  
end generate;
```

Example: outcome as multiple driven

GENERATE Shifter Example

```
library ieee;
use ieee.std_logic_1164.all;


entity GENERATE_as_Shifter is
port (input: in std_logic_vector (3 downto 0);
      sel: in integer range 0 to 4;
      output: out std_logic_vector (7 downto 0));
end GENERATE_as_Shifter;
architecture dataflow of GENERATE_as_Shifter is

subtype vector is std_logic_vector (7 downto 0);
type matrix is array (4 downto 0) of vector;
signal rowarray: matrix;
begin

rowarray(0) <= "0000" & input;
d: For i in 1 to 4 generate
    rowarray(i) <= rowarray(i-1) (6 downto 0) & '0';
end generate;
output <= rowarray(sel);
end dataflow;
```

```
Rowarray (0): 0 0 0 0 1 1 1 1
Rowarray (1): 0 0 0 1 1 1 1 0
Rowarray (2): 0 0 1 1 1 1 0 0
Rowarray (3): 0 1 1 1 1 0 0 0
Rowarray (4): 1 1 1 1 0 0 0 0
```

Fig: VHDL Code and Vector Waveform Output

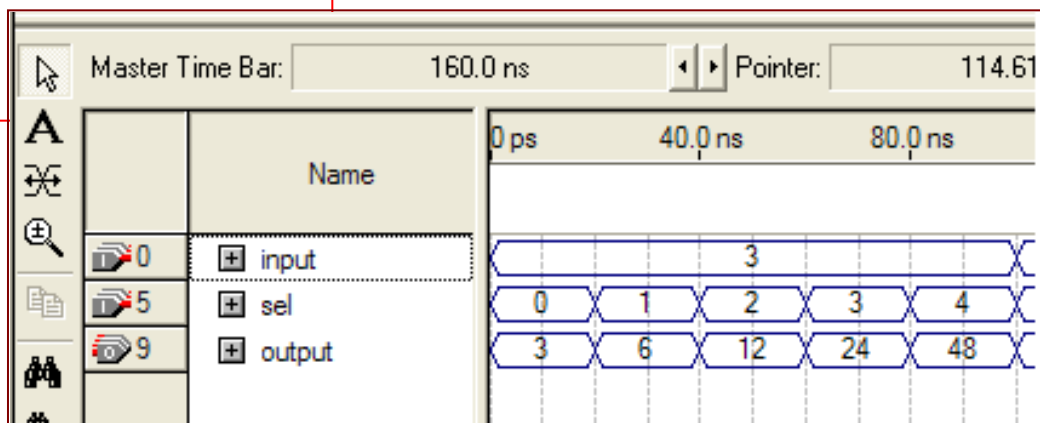

Home Work

PART-II: SEQUENTIAL CODE

Sequential Code

- VHDL is inherently concurrent
- IF, WAIT, CASE, and LOOP are executed inside the PROCESSES, FUNCTIONS, and PROCEDURES that are sequentially processed.
- Variable is not global, should be declared inside the process
- Signal can be used globally

Sequential statements: The Process

- A VHDL construct used for grouping sequential statements
- Statements are processed sequentially during simulation
- Can be either *active* or *inactive* during simulation
- A Process typically has a SENSITIVITY LIST except when WAIT is used

```
PROCESS (sensitivity list)  
-- optional variable declarations  
BEGIN  
           sequential statements  
END PROCESS ;
```

The Process Sensitivity List

- A Process is invoked when one or more of the signals within the sensitivity list change, e.g.

```
ARCHITECTURE archlist OF list IS
```

```
BEGIN
```

```
    nand0: PROCESS (a, b)
```

```
    BEGIN
```

```
        c <= NOT (a AND b) ;
```

```
    END PROCESS nand;
```

```
END archlist;
```

if either a or b changes in any way, the process is invoked

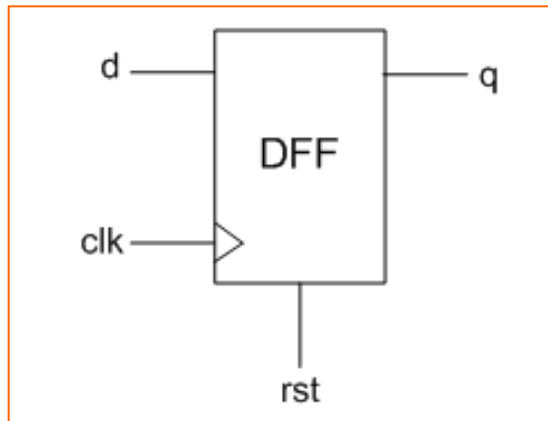


Fig: D Flip Flop Symbol

```

library ieee;
use ieee.std_logic_1164.all;


entity FFD is
port (d,clk,rst: in std_logic;
      q: out std_logic);
end FFD;

architecture behav of FFD is

begin
FlipFlop: process (clk,rst)
begin
    if (rst='1') then
        q<='0';
    elsif (clk'event and clk='1') then
        q<=d;
    end if;
end process;
end behav;


```

Fig: DFF Vector Waveform

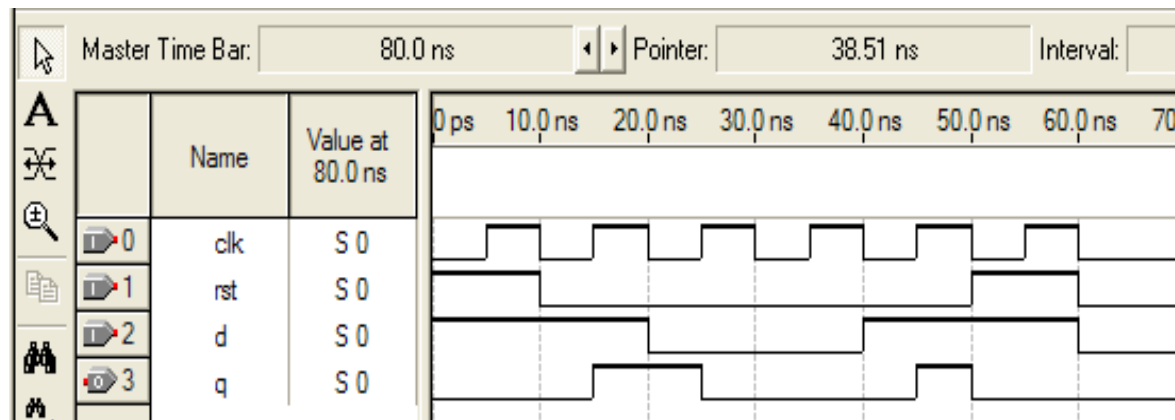


Signal Assignment in Processes
 
```
LIBRARY ieee;  
USE  
ieee.std_logic_1164.ALL;  
ENTITY mux2ltch IS PORT (  
    a, b: IN std_logic;  
    s, en: IN std_logic;  
    x: BUFFER std_logic);  
END mux2ltch;
```



Signal Assignment in Processes: Incorrect Solution
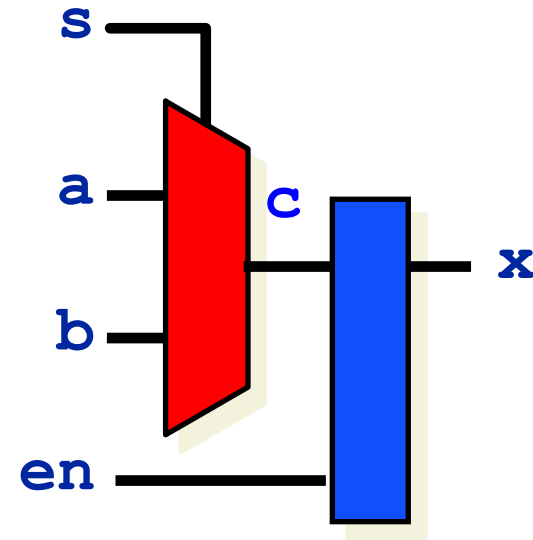
```
ARCHITECTURE archmux2ltch OF mux2ltch IS
    SIGNAL c: std_logic;
BEGIN
    mux: PROCESS (a,b,s,en)
    BEGIN
        IF s = '0' THEN c <= a;
        ELSE c <= b;
        END IF;
        x <= (x AND (NOT en)) OR (c AND en);
    END PROCESS mux; -- c is updated here!
END archmux2ltch;
```




PROCESS: A correct solution

```
ARCHITECTURE archmux2ltch OF mux2ltch IS  
    SIGNAL c: std_logic;  
BEGIN  
    mux: PROCESS (a, b, s)  
    BEGIN  
        IF s = '0' THEN c <= a;  
        ELSE c <= b;  
        END IF;  
    END PROCESS mux;    -- c is updated here!  
    x <= (x AND (NOT en)) OR (c AND en);  
END archmux2ltch;
```


IF Statement

 
```
IF condition THEN assignment;  
ELSIF condition THEN assignment;  
.....  
ELSE assignments;  
END IF;
```



Counter Example Code

```
library ieee;  
use ieee.std_logic_1164.all;  
entity counte_if is  
port (clk : in std_logic;  
      count : out integer range 0 to 9);  
end counte_if;  
architecture behav of counte_if is  
begin  
  countr: process (clk)  
    variable temp: integer range 0 to 10;  
  begin  
    if (clk'event and clk='1') then  
      temp:=temp+1;  
      if (temp=10) then temp:=0;  
      end if;  
    end if;  
    count<=temp;  
  end process;  
end behav;
```

Fig: Counter
Vector Waveform

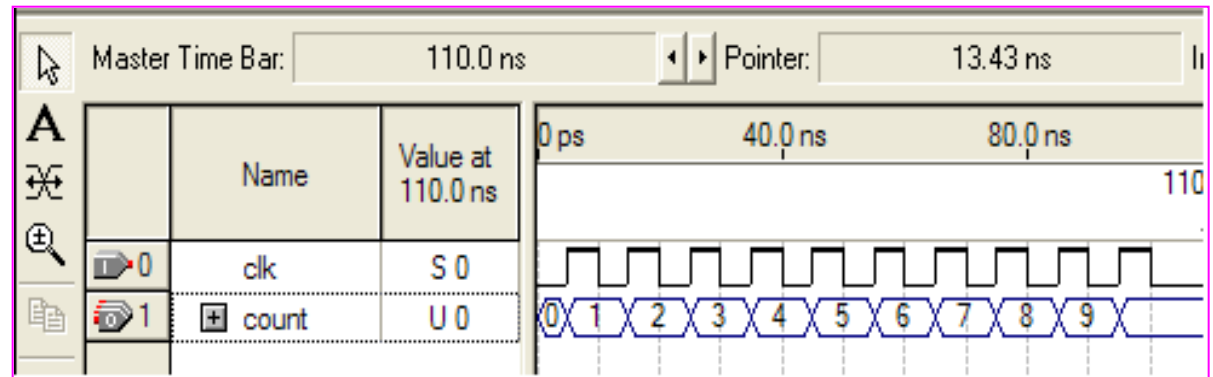

WAIT

```
-- WAIT Statement Syntax
Wait until signal_condition;
Wait on signal [signal1, signal2, ...];
wait for time;
```

- No sensitivity list required
- WAIT UNTIL accepts one signal, WAIT ON accepts multiple, Wait For is only for simulation purpose
- Do yourself – develop DFF code using wait on instead of IF only, and simulate it in Quartus-II, verify the functionality and observe the area-performance differences .

```
-- WAIT Untill Sample Code

waitS: Process -- no sensitiviuy list
begin
    wait untill (clk'event and clk='1');
    if (reset='1') then
        otpt<="00000000";
    elsif (clk'event and clk='1') then
        otpt<= input;
    end if;
end process;

--Wait On Sample Code
waitS: Process
begin
    wait on clk, reset;
    if (reset = '1') then
        otpt<="00000000";
    elsif (clk'event and clk='1') then
        otpt<=input;
    end if;
end process;
```

CASE

DFF with CASE Statement

--CASE Syntax

```
CASE identifier is
WHEN value => assignments;
WHEN value => assignments;
  ..
END case;
```

--CASE sample Code

```
CASE sel is
when "00" => x <=a; y<=b;
When "01" => x <=b; y<=c;
when others
```

- CASE statement has resemblance with WHEN
- Unlike WHEN, CASE allows multiple assignments

```
Entity DFF_case is
port (d,clk,rst: in std_logic;
      q: out std_logic);
end DFF_case;
architecture behav of DFF_case is
begin
process (clk,rst)
begin
case rst is
when '1' => q <= '0';
when '0' =>
if (clk'event and clk='1') then
q<=d;
end if;
when others=> NULL;
end case;
end process;
end behav;
```

LOOP: FOR and WHILE

```
--FOR LOOP Syntax
```

```
label: FOR identifier In range Loop  
    (sequential statements)  
end Loop [label];
```

```
-- WHILE LOOP Syntax
```

```
label: WHILE condition LOOP  
    (sequential statements)  
end Loop [label];
```

```
--EXIT Syntax
```

```
label: EXIT [label] [WHEN condition]
```

```
-- NEXT Syntax
```

```
label: NEXT [loop_label] [WHEN condition];
```

Sample Example Codes

```
--Example for FOR/LOOP
```

```
FOR i in 7 downto 0 LOOP  
  a(i) <= enable AND t(i+2);  
  r(0,i) <= t(i);  
end Loop;
```

```
--Example code EXIT
```

```
d: for i in sample'range loop  
  case sample (i) is  
    when '0' => count:=count+1;  
    when others => exit;  
  end case;  
end loop;
```

```
--Example code WHILE
```

```
While (i<5) loop  
  wait untill clock'event and clock='1';  
  (other statements)  
end loop;
```

```
--Example Code NEXT
```

```
g: for i in 7 downto 0 loop  
  next when i=skip;  
  (.....)  
end loop;
```

CASE Versus IF and WHEN

- CASE and IF allows selection of one sequence of statements for execution from a number of alternative sequences
- CASE vs WHEN
 - CASE is sequential, while WHEN is concurrent
 - CASE can only be used inside the process, FUNCTIONS, or PROCEDURES while WHEN outside is reverse
 - All permutations can be tested by both
 - WHEN can have any number of assignments per test, while CASE is limited to only one
 - NULL is the keyword for no-action in CASE, Unaffected is used in WHEN for no-action (shown previously in examples)

END OF THE LECTURE

Lecture 9 & 10